

ASSIGNMENT 7: CIRCUIT ANALYSIS USING SYMPY AND LAPLACE TRANSFORMS

Nithin Babu [EE18B021]

April 6, 2022

Abstract

The goal of this assignment is the following:

- To analyze Filters using Laplace Transform.
- To see how python can be used for symbolic Algebra.
- To plot graphs to understand high pass and low pass analog filters.

Low Pass Filter

The low pass filter that we use gives the following matrix equation after simplification of the modified nodal equations.

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{1}{1+sR_2C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -\frac{1}{R_1} - \frac{1}{R_2} - sC_1 & \frac{1}{R_2} & 0 & sC_1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)/R_1 \end{pmatrix}$$

The python code snippet that declares the low pass function and solves the matrix equation to get the V matrix is as shown below:

```
def lowpass_filter(R1,R2,C1,C2,G,Vi):  
    A=Matrix([[0,0,1,-1/G],[-1/(1+s*R2*C2),1,0,0],[0,-G,G,1],[-1/R1-1/R2-s*C1,1/R2,  
    b=Matrix([0,0,0,Vi/R1])  
    v=A.inv()*b  
    return A,b,v
```

The plot for the magnitude of the transfer function (magnitude bode plot) is as shown below:

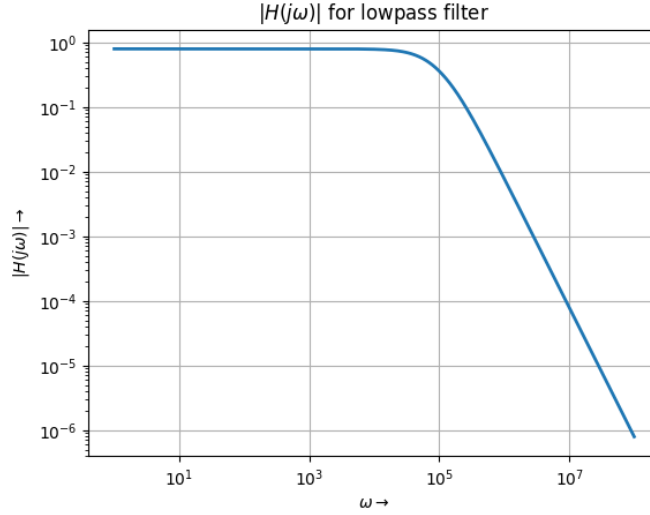


Figure 1: Magnitude bode plot of the low pass filter

High Pass Filter

The high pass filter we use gives the following matrix equations after simplification of the modified nodal equations

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{sR_3C_2}{1+sR_3C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -1 - (sR_1C_1) - (sR_3C_2) & sC_2R_1 & 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)sR_1C_1 \end{pmatrix}$$

The python code snippet that declares the high pass function and solves the matrix equation to get the V matrix is as shown below:

```
def highpassfilter(R1,R2,C1,C2,G,Vi):
    A = Matrix([[0,0,1,-1/G],[-s*C2,(1/R2) +s*C2,0,0],[0,-G,G,1],[0-s*C1-s*C2-1/R1,s,0,0]])
    b = Matrix([0,0,0,Vi*s*C1])
    v=A.inv()*b
    return A,b,v
```

The plot for the magnitude of the transfer function (magnitude bode plot) is as shown below:

Format Change of Sympy Functions

The sympy functions, that are expressed in terms of 's', must be converted to another form that is understood by sp.signal. This is done using the

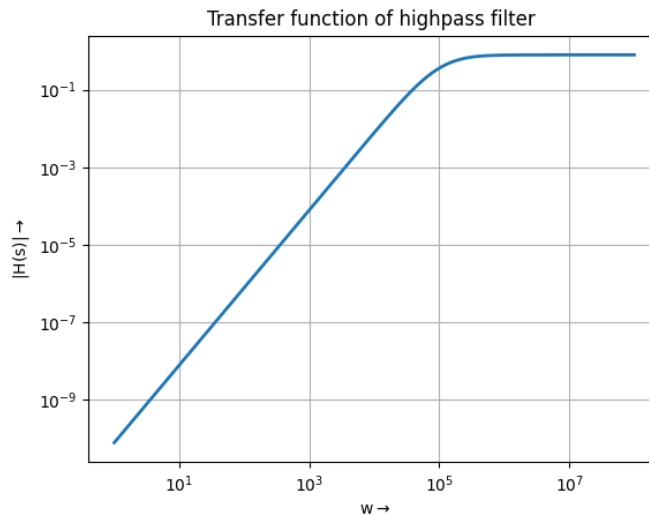


Figure 2: Magnitude bode plot of the high pass filter

sympytotransfrfunc() function.

The python code snippet is as shown:

```
def sympy_to_trnsfrfunc(func):
    num, den = simplify(func).as_numer_denom()
    num_list=Poly(num).all_coeffs()
    num_list = array(num_list, dtype='double')
    den_list=Poly(den).all_coeffs()
    den_list = array(den_list, dtype='double')
    h_lowpass=sp.lti(num_list,den_list)
    return h_lowpass
```

Step Response Of the Low Pass Filter

In order to find the step response of the low pass filter, we need to assign $V_i(s) = 1/s$. The python code below explains it.

```
h_lowpass=sympy_to_trnsfrfunc(H)
```

```
t=linspace(0,0.001,1000)
c=heaviside(t,0)
t,y,svec=sp.lsim(h_lowpass,c,t)
plt.plot(t,c,label='V_input')
plt.plot(t, y,label='V_output')
xlabel("t"+"$\\rightarrow$")
ylabel("V"+"$\\rightarrow$")
```

```

title("step response of the circuit")
grid(True)
legend()
show()

```

The plot for the step response of the low pass circuit is as shown:

 


Figure 3: Step response of low pass filter.

Response to Sum Of Sinusoids

When the input is a sum of sinusoids like,

$$V_i(t) = (\sin(2000\pi t) + \cos(2 * 10^6 \pi t)) u_o(t) \text{ Volts}$$

Then the output response for the lowpass filter can easily be found as shown in the code snippet.

```

t=linspace(0,0.001,1000)
Vi = np.multiply((np.sin(2000*np.pi*t)+np.cos(2000000*np.pi*t)),np.heaviside(t,1))
t,y,svec=sp.lsim(h_lowpass,Vi,t)
plt.plot(t,Vi,label='V_input')
plt.plot(t,y,label='V_output')
xlabel("t"+"$\rightarrow$")
ylabel("V"+"$\rightarrow$")
title("response of the circuit to vi(t) =(sin(2000t)+cos(2*10^6t))*u(t)")
plt.grid(True)
legend()

```

```
show()
show()
```

The output response to the sum of sinusoids for the low pass filter is as shown:

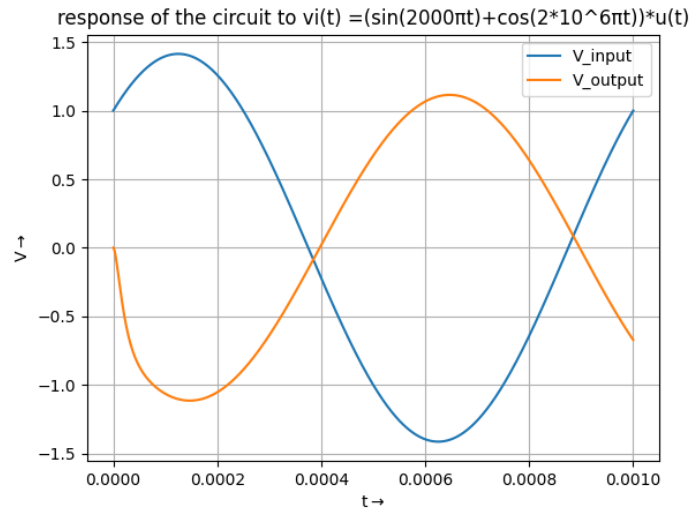


Figure 4: Output response to the sum of sinusoids.

Response to Damped Sinusoids

In this case we assign the input voltage as a damped sinusoid like,
Low frequency,

$$V_i(t) = e^{-0.5t}(\cos(2\pi t))u_o(t) \text{ Volts}$$

High frequency,

$$V_i(t) = e^{-5000t}(\cos(2 * 10^4 \pi t))u_o(t) \text{ Volts}$$

The code and plot of output responses for both cases in a high pass filter is as shown:

```
t=linspace(0,10,10000)
vi = np.multiply(np.multiply(np.exp(-0.5*t),np.sin(2*np.pi*t)),np.heaviside(t,0.5))
plt.plot(t,vi,label='V_input')
t,y,svec=sp.lsim(h_highpass,vi,t)
title("vo when vi is sinusoidal deacying")
plt.plot(t,y,label='V_output')
title("response of the circuit at low w ")
```

```

xlabel("t"+"$\rightarrow$")
ylabel("V"+"$\rightarrow$")
grid(True)
legend()
show()

t=linspace(0,0.001,10000)
vi = np.multiply(np.multiply(np.exp(-5000*t),np.sin(2*np.pi*1e4*t)),np.heaviside(t,0))
plt.plot(t,vi,label='V_input')
t,y,svec=sp.lsim(h_highpass,vi,t)
plt.plot(t,y,label='V_output')
title("response of the circuit at high w ")
xlabel("t"+"$\rightarrow$")
ylabel("V"+"$\rightarrow$")
plt.grid(True)
legend()
show()

```

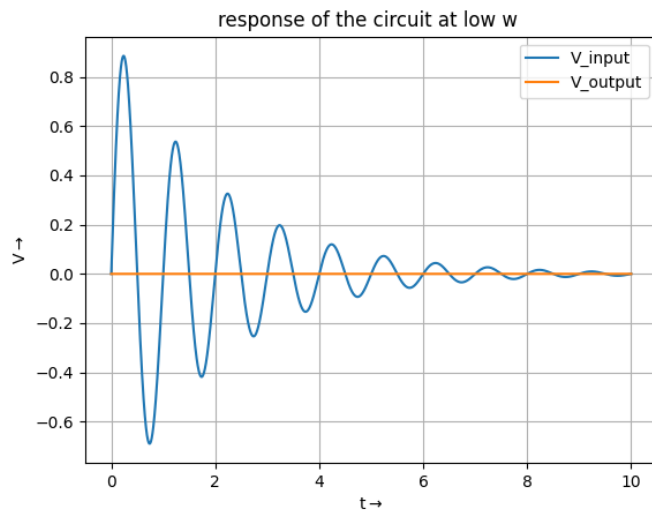


Figure 5: Output response of a high frequency damped sinusoid

Step Response of High Pass Filter

In order to find the step response of the high pass filter, we need to assign $V_i(s) = 1/s$. The python code below explains it.

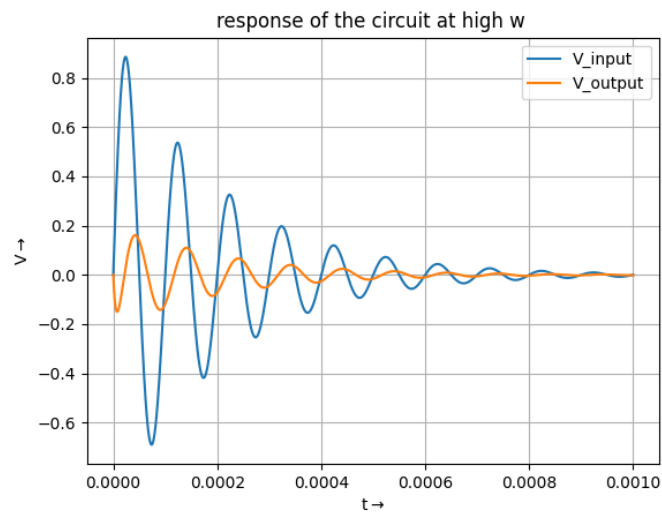


Figure 6: Output response of a low frequency damped sinusoid

```
t=linspace(0,0.001,10000)
vi=heaviside(t,0)
plt.plot(t,vi,label='V_input')
t,y,svec=sp.lsim(h_highpass,vi,t)
plt.plot(t,y,label='V_output')
xlabel("t"+"$\\rightarrow$")
ylabel("V"+"$\\rightarrow$")
title("step response of the circuit")
plt.grid(True)
legend()
show()
```

The plot of the step response for a high pass filter is as shown:

 


Figure 7: Step response for a high pass filter

The unit step response, as expected is high at $t=0$ when there is an abrupt change in the input. Since there is no other change at large time values outside the neighbourhood of 0, the Fourier transform of the unit step has high values near 0 frequency, which the high pass filter attenuates.

Conclusion

In conclusion, the sympy module has allowed us to analyse quite complicated circuits by analytically solving their node equations. We then interpreted the solutions by plotting time domain responses using the signals toolbox. Thus, sympy combined with the scipy.signal module is a very useful toolbox for analyzing complicated systems like the active filters in this assignment.